

CE203/SC301 Tutorial 2: Measurement System - Filters

- 1) Figure Q1 shows a simple op-amp high pass filter (HPF). It is proposed to use the filter to pass all signals above 1KHz, with a passband gain of 26db. The Op-amp has a gain-bandwidth product of 1MHz.
- Design a suitable HPF based on the given filter topology.
 - Sketch the frequency response of the filter. (Hint: consider the limited gain-bandwidth product of the Op-amp). How does this HPF perform relative to an ideal HPF ?
 - Estimate the input impedance of the filter at 25KHz.
 - Design another suitable HPF based passive RC network and sketch the frequency response. Contrast the responses from the two filters.

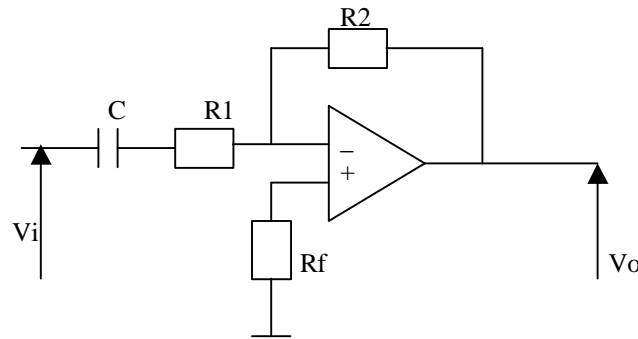


Figure Q1

- 2) In biomedical measurement system that measures the "electrical wave pattern" of a patient. The signal called EEG (Electroencephalogram) has a magnitude of $50\mu\text{V}$ at a frequency range of 0.5 to 25 Hz is needed in the data analysis of the neural pattern. Disturbances (noise interferences) from the muscles called EMG (Electromyogram) with an amplitude of $100\mu\text{V}$ at 100Hz-3000Hz as well as from EMI (Electromagnetic interference) with a noise level of 10mV at 50Hz are present in the measurement system. To effectively retrieve the required signal, EEG, the noise should be reduced to a magnitude of not more than $1\mu\text{V}$. The feasibility of applying low pass filtering to condition the signal for analysis has to be investigated.
- Use $1\mu\text{V}$ as the reference, sketch the signal and noise spectrum.
 - Hence, establish the required attenuation necessary to achieve the required signal conditioning.
 - Determine the order of the filter needed.
 - How would you reduce the order of the LPF needed?
 - Design a suitable Butterworth LPF to meet the requirement using the equal component value Sallen-Key topology. What is the magnitude of the passband EEG signal at the output of the filter.